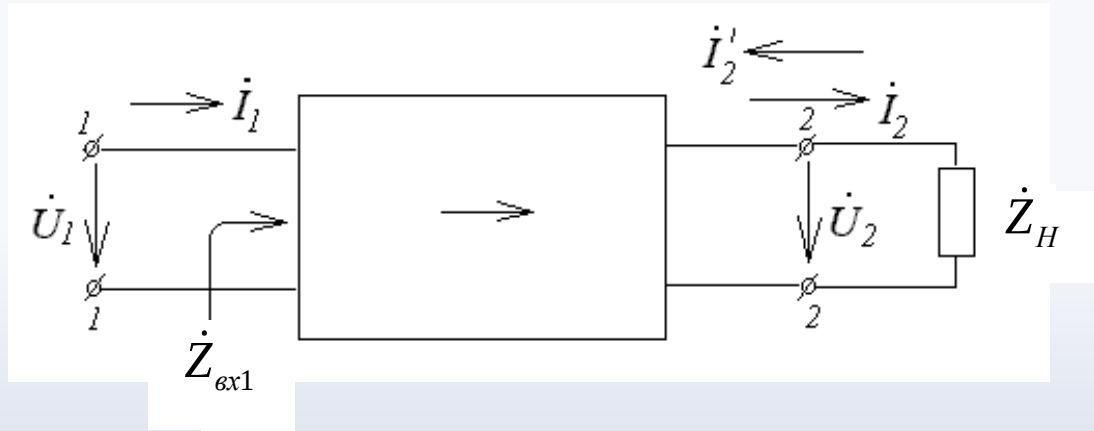


ЭЛЕКТРОТЕХНИКА

Лектор:


к.ф.-м.н. Алимгазинова Назгуль Шакаримовна

Входные сопротивления четырехполюсника



$$\dot{Z}_{ex1} = \frac{\dot{U}_1}{\dot{I}_1}$$

a)

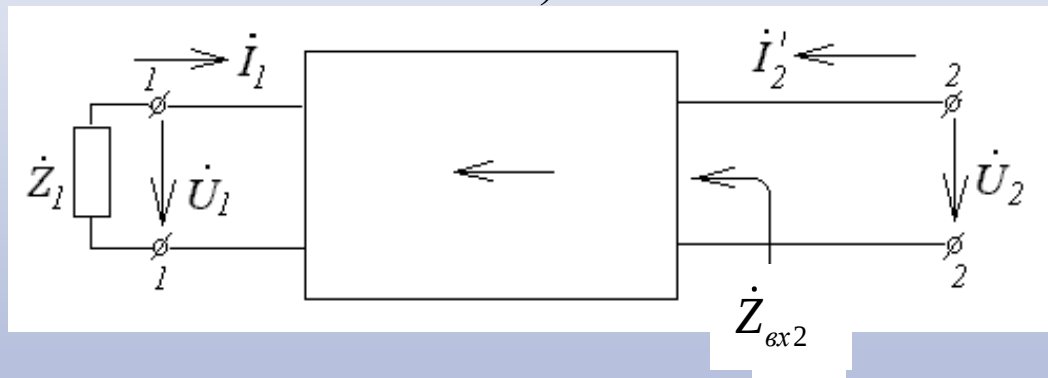

$$\dot{Z}_{ex2} = \dot{Z}_{ex} = \frac{\dot{U}_2}{\dot{I}'_2}$$

б)

$$\dot{Z}_{ex1} = \frac{\dot{U}_1}{\dot{I}_1} = \frac{\dot{A}_{11}\dot{U}_2 + \dot{A}_{12}\dot{I}_2}{\dot{A}_{21}\dot{U}_2 + \dot{A}_{22}\dot{I}_2} = \frac{\dot{A}_{11}\dot{Z}_H + \dot{A}_{12}}{\dot{A}_{21}\dot{Z}_H + \dot{A}_{22}}, \quad \dot{Z}_H = \dot{U}_2 / \dot{I}_2$$

$$\dot{Z}_{1XX} = \frac{\dot{A}_{11}}{\dot{A}_{21}}, \quad Z_{1K3} = \frac{\dot{A}_{12}}{\dot{A}_{22}}$$

$$\dot{Z}_{2XX} = \frac{\dot{A}_{22}}{\dot{A}_{21}}, \quad Z_{2K3} = \frac{\dot{A}_{12}}{\dot{A}_{11}}$$

$$\dot{Z}_{ex1} = \frac{\dot{A}_{11}}{\dot{A}_{21}} \frac{\frac{\dot{A}_{12}}{\dot{A}_{11}} + \dot{Z}_H}{\frac{\dot{A}_{22}}{\dot{A}_{21}} + \dot{Z}_H} = \dot{Z}_{1XX} \frac{\dot{Z}_{2K3} + \dot{Z}_H}{\dot{Z}_{2XX} + \dot{Z}_H},$$

$$\dot{Z}_{ex2} = \dot{Z}_{2XX} \frac{\dot{Z}_{1K3} + \dot{Z}_1}{\dot{Z}_{1XX} + \dot{Z}_1}$$

Характеристические параметры

(вторичные)

$\dot{Z}_i$ - внутреннее сопротивление генератора,
 $\dot{Z}_H$ - сопротивление нагрузки

Если $\begin{cases} \dot{Z}_i = \dot{Z}_{\text{ex1}} \\ \dot{Z}_{\text{ex2}} = \dot{Z}_H \end{cases}$ согласованный режим 4П

$$\dot{Z}_{\text{ex1}} = \frac{\dot{A}_{11}\dot{Z}_H + \dot{A}_{12}}{\dot{A}_{21}\dot{Z}_H + \dot{A}_{22}} = \dot{Z}_i, \quad \dot{Z}_{\text{ex2}} = \frac{\dot{A}_{22}\dot{Z}_1 + \dot{A}_{12}}{\dot{A}_{21}\dot{Z}_1 + \dot{A}_{11}} = \dot{Z}_H.$$

Характеристические сопротивления

$$\dot{Z}_{\text{ex1}} = \dot{Z}_i = \dot{Z}_{1C}$$

$$\dot{Z}_{\text{ex2}} = \dot{Z}_H = \dot{Z}_{2C}$$

$$\dot{Z}_{1C} = \frac{\dot{A}_{11}\dot{Z}_{2C} + \dot{A}_{12}}{\dot{A}_{21}\dot{Z}_{2C} + \dot{A}_{22}}, \quad \dot{Z}_{2C} = \frac{\dot{A}_{22}\dot{Z}_{1C} + \dot{A}_{12}}{\dot{A}_{21}\dot{Z}_{1C} + \dot{A}_{11}}.$$

$$\dot{Z}_{1C} = \sqrt{\frac{\dot{A}_{11}\dot{A}_{12}}{\dot{A}_{21}\dot{A}_{22}}}, \quad \dot{Z}_{2C} = \sqrt{\frac{\dot{A}_{22}\dot{A}_{12}}{\dot{A}_{21}\dot{A}_{11}}}.$$

$$\frac{\dot{A}_{11}}{\dot{A}_{21}} = \dot{Z}_{1XX}, \quad \frac{\dot{A}_{12}}{\dot{A}_{22}} = \dot{Z}_{1K3}, \quad \frac{\dot{A}_{22}}{\dot{A}_{21}} = \dot{Z}_{2XX}, \quad \frac{\dot{A}_{12}}{\dot{A}_{11}} = \dot{Z}_{2K3}$$

$$\dot{Z}_{1C} = \sqrt{\dot{Z}_{1XX}\dot{Z}_{1K3}}, \quad \dot{Z}_{2C} = \sqrt{\dot{Z}_{2XX}\dot{Z}_{2K3}}.$$

Если 4П согласован с нагрузкой

$$\dot{Z}_H = \frac{\dot{U}_2}{\dot{I}_2} = \dot{Z}_{2C} = \sqrt{\frac{\dot{A}_{22}\dot{A}_{12}}{\dot{A}_{21}\dot{A}_{11}}},$$

$$\begin{cases} \dot{U}_1 = \dot{A}_{11}\dot{U}_2 + \dot{A}_{12}\frac{\dot{U}_2}{\dot{Z}_{2C}}, \\ \dot{I}_1 = \dot{A}_{21}\dot{Z}_{2C}\dot{I}_2 + \dot{A}_{22}\dot{I}_2. \end{cases} \Rightarrow \begin{cases} \dot{U}_1 = \dot{U}_2 \left(\dot{A}_{11} + \sqrt{\frac{\dot{A}_{12}\dot{A}_{21}\dot{A}_{11}}{\dot{A}_{22}}} \right), \\ \dot{I}_1 = \dot{I}_2 \left(\dot{A}_{22} + \sqrt{\frac{\dot{A}_{12}\dot{A}_{21}\dot{A}_{22}}{\dot{A}_{11}}} \right). \end{cases}$$

$$\begin{cases} \frac{\dot{U}_1}{\dot{U}_2} \cdot \sqrt{\frac{\dot{A}_{22}}{\dot{A}_{11}}} = \sqrt{\dot{A}_{11}\dot{A}_{22}} + \sqrt{\dot{A}_{12}\dot{A}_{21}}, \\ \frac{\dot{I}_1}{\dot{I}_2} \cdot \sqrt{\frac{\dot{A}_{11}}{\dot{A}_{22}}} = \sqrt{\dot{A}_{11}\dot{A}_{22}} + \sqrt{\dot{A}_{12}\dot{A}_{21}}. \end{cases}$$

$$\sqrt{\frac{\dot{A}_{11}}{\dot{A}_{22}}} = \sqrt{\frac{\dot{Z}_{1C}}{\dot{Z}_{2C}}} = n_T$$

**Коэффициент
трансформации**

Входное сопротивление согласованного 4П

$$\dot{Z}_{\text{ex1}} = \dot{Z}_{1C} = n_T^2 \dot{Z}_{2C} = n_T^2 \dot{Z}_H,$$

g – постоянная передачи

$$\frac{1}{n_T} \frac{\dot{U}_1}{\dot{U}_2} = n_T \frac{\dot{I}_1}{\dot{I}_2} = \sqrt{\dot{A}_{11} \dot{A}_{22}} + \sqrt{\dot{A}_{12} \dot{A}_{21}} = e^g$$

Для симметричного 4П $\dot{A}_{11} = \dot{A}_{22}$, $\dot{Z}_{1C} = \dot{Z}_{2C}$, $n_T = 1$,

$$g = \ln \frac{\dot{U}_1}{\dot{U}_2} = \ln \frac{\dot{I}_1}{\dot{I}_2} = \ln \left(\sqrt{\dot{A}_{11} \dot{A}_{22}} + \sqrt{\dot{A}_{12} \dot{A}_{21}} \right),$$

В случае согласованности с нагрузкой

$$\begin{cases} \dot{Z}_H = \dot{Z}_{2C}, \\ \dot{Z}_{2C} \dot{I}_2 = \dot{U}_2, \\ chg + shg = e^g \end{cases} \begin{cases} \dot{U}_1 = \sqrt{\frac{\dot{Z}_{1C}}{\dot{Z}_{2C}}} \dot{U}_2 e^g, \\ \dot{I}_1 = \sqrt{\frac{\dot{Z}_{2C}}{\dot{Z}_{1C}}} \dot{I}_2 e^g \end{cases}$$

Постоянная передачи

$$g = a + jb.$$

$$\begin{aligned}\dot{U}_1 &= |\dot{U}_1| e^{j\varphi_{U1}}, & \dot{U}_2 &= |\dot{U}_2| e^{j\varphi_{U2}}, & \dot{Z}_{1C} &= |\dot{Z}_{1C}| e^{j\varphi_{1C}}, \\ \dot{I}_1 &= |\dot{I}_1| e^{j\varphi_{I1}}, & \dot{I}_2 &= |\dot{I}_2| e^{j\varphi_{I2}}, & \dot{Z}_{2C} &= |\dot{Z}_{2C}| e^{j\varphi_{2C}}.\end{aligned}$$

$$\left\{ \begin{aligned} |\dot{U}_1| e^{j\varphi_{U1}} &= \left[\sqrt{\frac{|\dot{Z}_{1C}|}{|\dot{Z}_{2C}|}} |\dot{U}_2| e^a \right] e^{j\varphi_{U2}} e^{j\frac{1}{2}(\varphi_{1C} - \varphi_{2C})} e^{jb}, \\ |\dot{I}_1| e^{j\varphi_{I1}} &= \left[\sqrt{\frac{|\dot{Z}_{2C}|}{|\dot{Z}_{1C}|}} |\dot{I}_2| e^a \right] e^{j\varphi_{I2}} e^{j\frac{1}{2}(\varphi_{2C} - \varphi_{1C})} e^{jb}. \end{aligned} \right.$$

$$\varphi_{U1} - \varphi_{U2} = \frac{1}{2}(\varphi_{1C} - \varphi_{2C}) + jb, \quad \varphi_{I1} - \varphi_{I2} = \frac{1}{2}(\varphi_{2C} - \varphi_{1C}) + jb.$$

Для симметричного 4П

$$\begin{cases} |\dot{U}_1| e^{j\varphi_{U1}} = |\dot{U}_2| e^a e^{j\varphi_{U2}} e^{jb}, \\ |\dot{I}_1| e^{j\varphi_{I1}} = |\dot{I}_2| e^a e^{j\varphi_{I2}} e^{jb}. \end{cases}$$

b - коэффициент фазы (радиан или градус):

$$b = \varphi_{U1} - \varphi_{U2} = \varphi_{I1} - \varphi_{I2}.$$

a – собственный коэффициент затухания:

$$a = \ln \frac{|\dot{U}_1|}{|\dot{U}_2|} = \ln \frac{|\dot{I}_1|}{|\dot{I}_2|} \quad (\text{непер}).$$

$$a(\text{бел}) = \lg \frac{U_1 I_1}{U_2 I_2} = \lg \frac{S_1}{S_2}.$$

$$\frac{S_1}{S_2} = \frac{U_1^2}{U_2^2} = \frac{I_1^2}{I_2^2} \quad \longrightarrow \quad a(\text{бел}) = 2 \lg \frac{U_1}{U_2} = 2 \lg \frac{I_1}{I_2}.$$

$$a(\text{дб}) = 20 \lg \frac{U_1}{U_2} = 20 \lg \frac{I_1}{I_2} = 10 \lg \frac{S_1}{S_2}.$$

$$1 \text{ дб} \approx 0,115 \text{ нел}; \quad 1 \text{ нел} \approx 8,7 \text{ дб}.$$